

NEW IDEAS FOR
VERY SIMPLE SOFTWARE-DEFINED DSB RADIOS
by Eduardo Alonso, EA3GHS
<http://ea3ghs.googlepages.com>

It's possible to build very simple and didactic receivers if you use a personal computer as a intermediate frequency amplifier and filter. With simple circuits is possible to see that each component makes and what gain/losses has every stage. Also, it's more simple simulate with SPICE/APLAC.





Reviewing my "Very Simple SDR DSB RX" circuit again,

1) I am not happy that the adjustable resistor moves the bias point of the diode and the oscillator level simultaneously. A possible solution is the circuit (a).

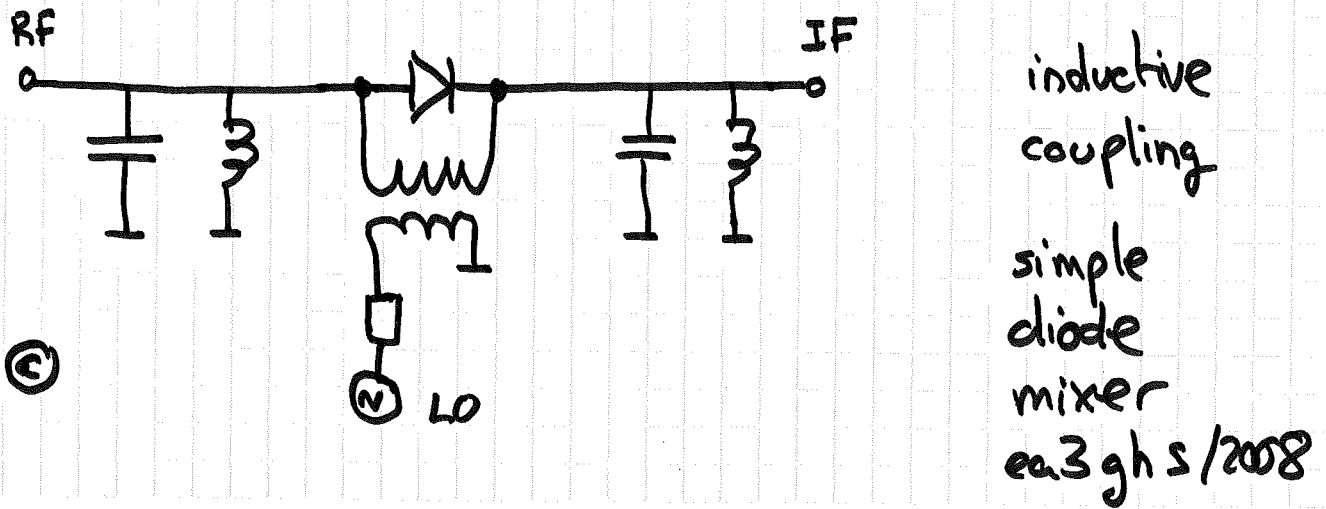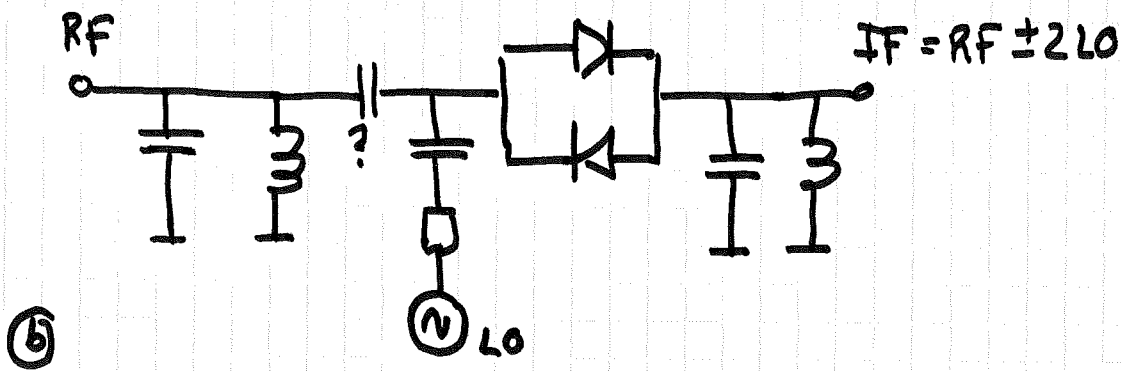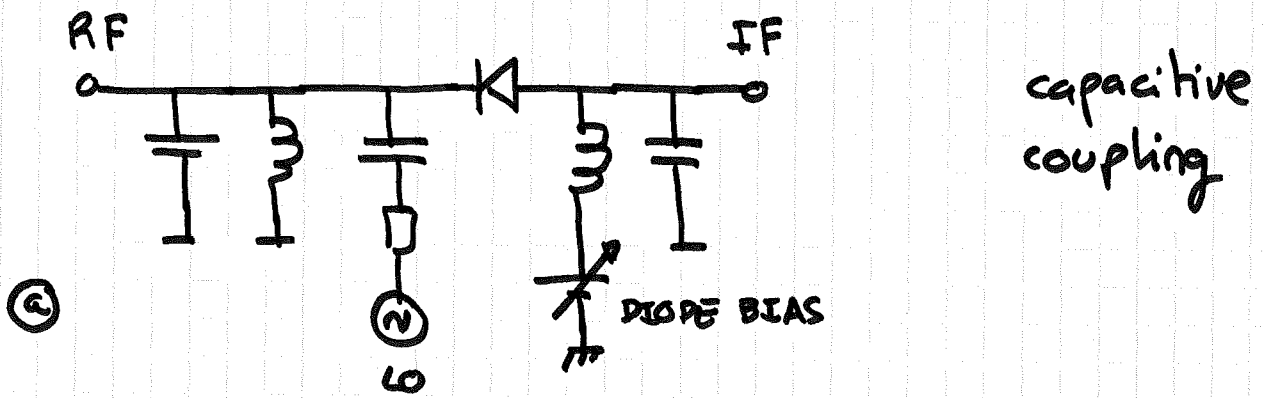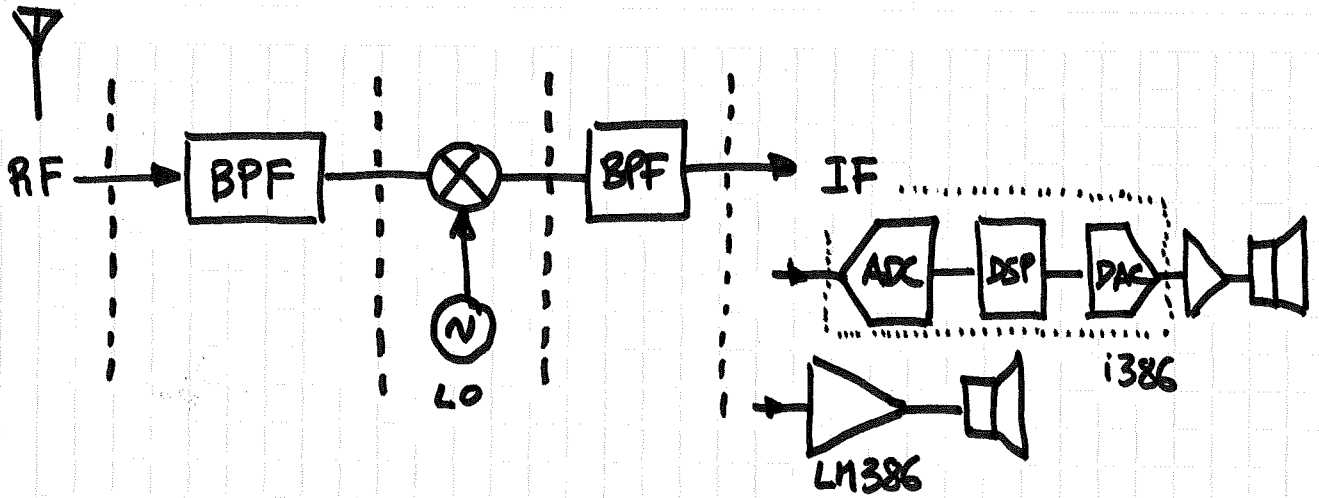
2) Is possible to build a lot of other simple circuits changing only the mixer. The oscillator and input (RF preselector) and output (ADC anti-aliasing) filter can be the same. See the attached figures. There are ideas to be tested.

I am very happy with the circuits (c) "simple diode mixer" and (d) "double diode doubler mixer".

The impedance adaptation between each stage must be checked. These circuits have not gain, and then they should have small losses !! Maybe the circuit (i) is a low cost solution..




①

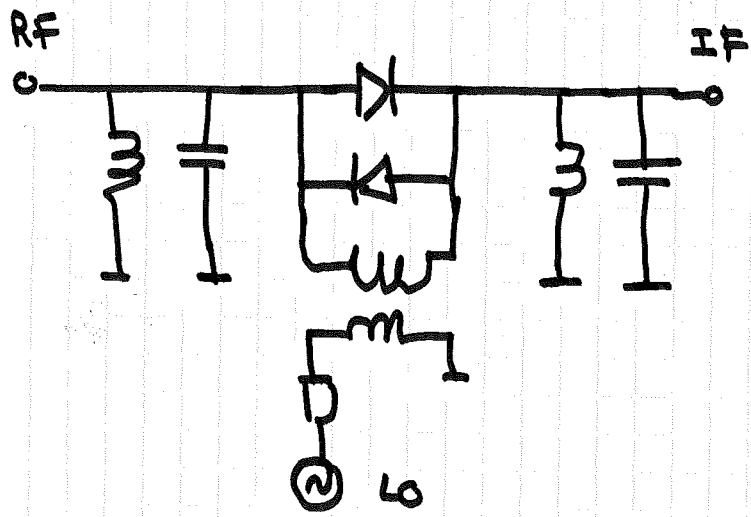


double
diode
doubler
mixer

②


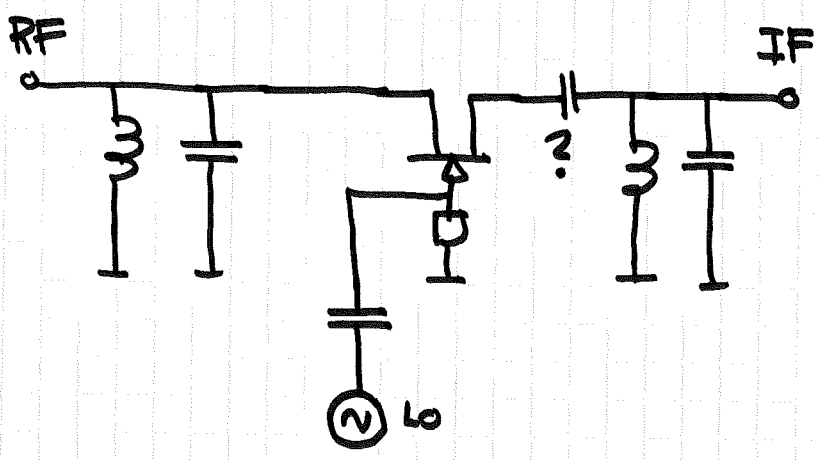


FET
as
switcher


③

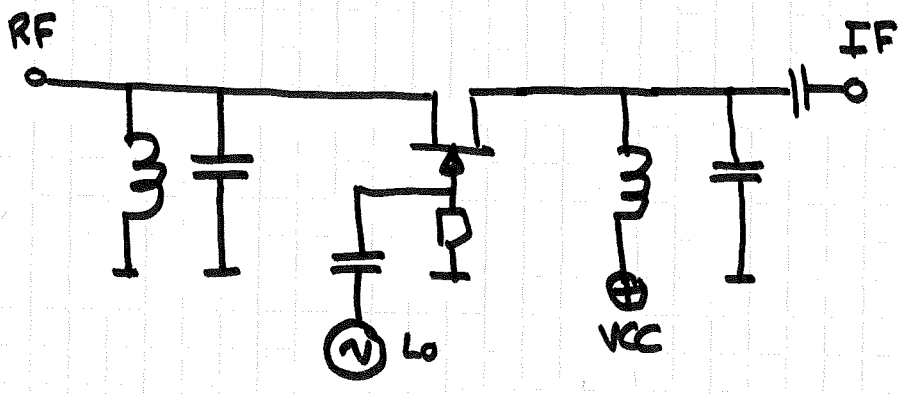

FET
as
non-linear
amplifier

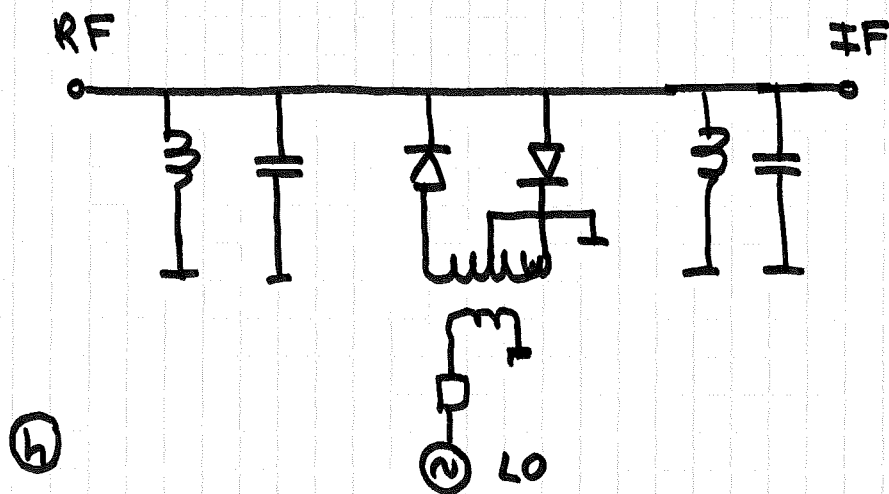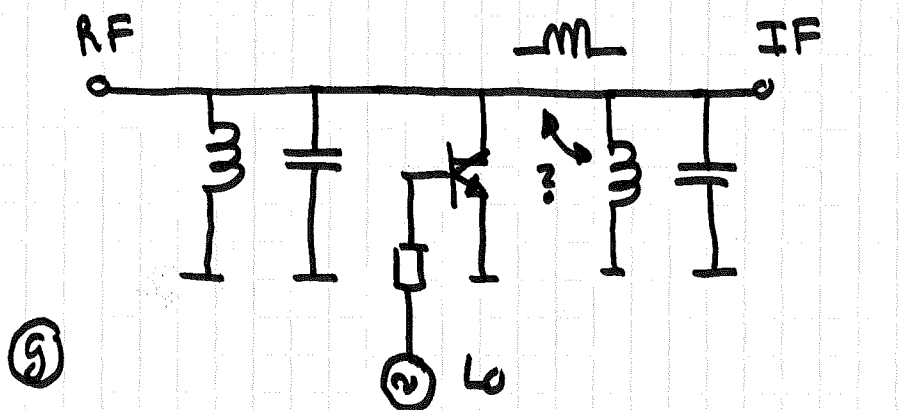


SOUND CARD ADC

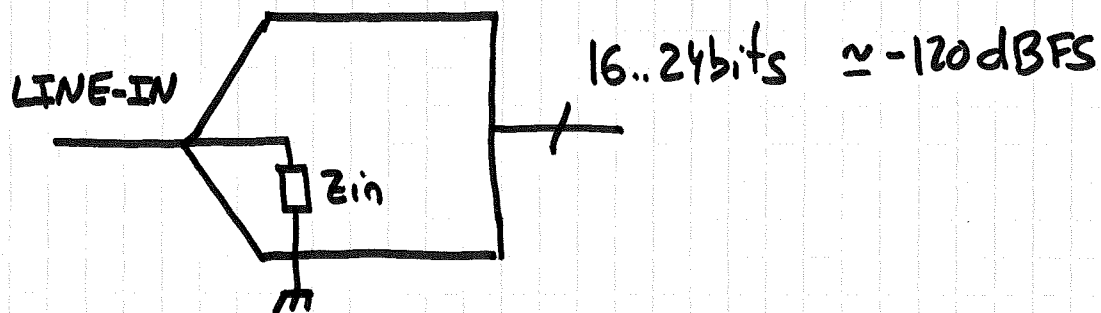

Z_{in} not well defined, $Z_{in} \approx 10k\Omega$


$$V_{MAX} = 1V_{RMS} = 2.8V_{p-p}$$

$$1V_{RMS} @ 1k\Omega = 0dBm = 0dBFS$$

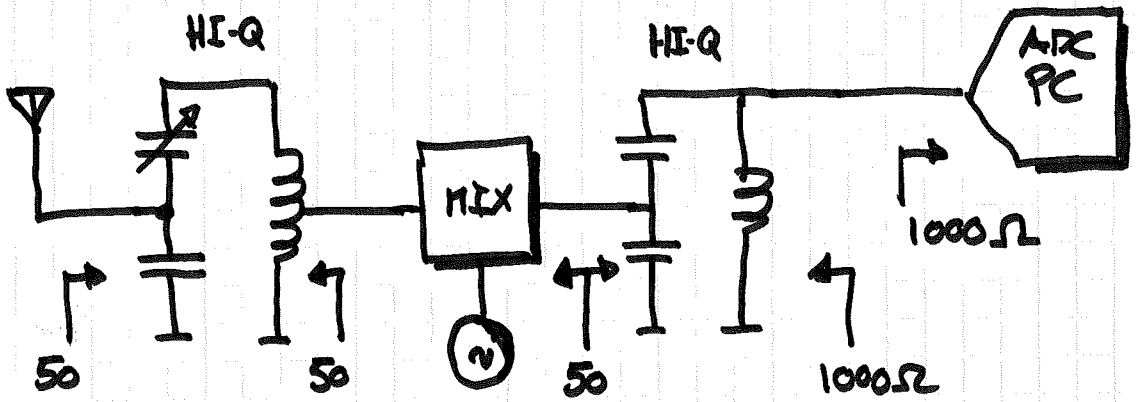


using capacitive transformers to match stages

(i)

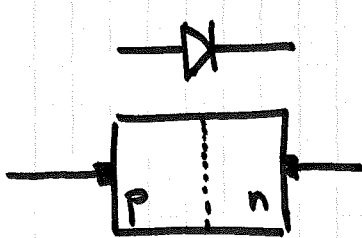

diode

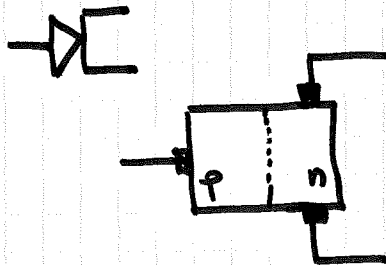

jet = diode with 3 terminals

